

# The NOvA APD Readout Chip


Tom Zimmerman

Fermilab


May 19, 2006
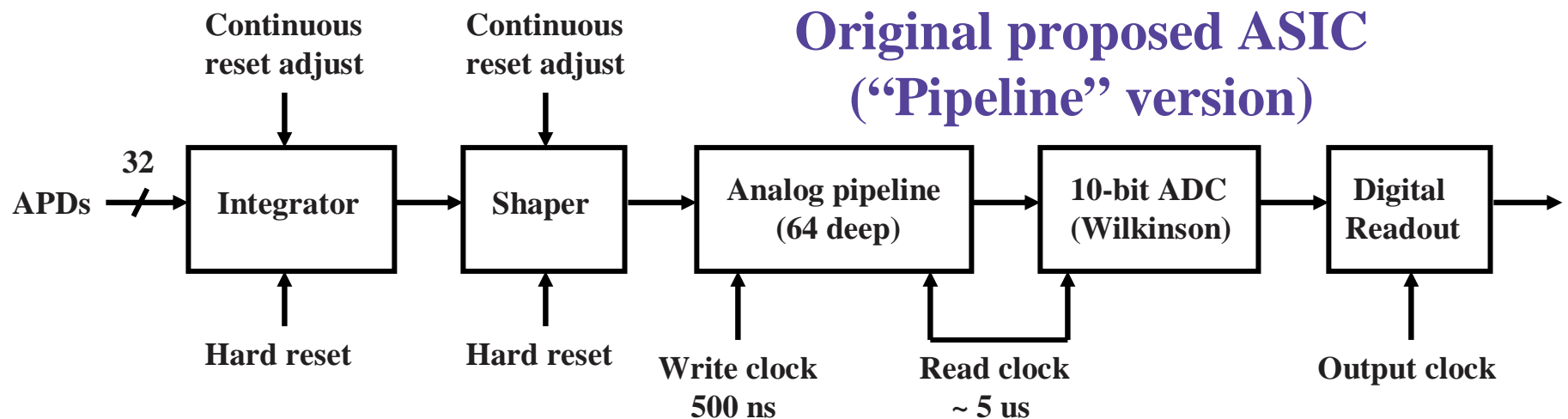
# NOvA Detector Readout Requirements

- Record neutrino signal from detector APDs (APD gain  $\sim 100$ ,  $C \sim 10\text{pF}$ )
- MIP  $\sim 25$  pe gives 2500e input signal
- Need low noise front end ( $< 200$  e)
- 10  $\mu\text{s}$  long beam spill every 2 seconds
- Beam spill arrival known to  $\pm 10$   $\mu\text{s}$
- Integrate APD signals in 500 ns buckets during a 30  $\mu\text{s}$  window
- After acquisition, perform Dual Correlated Sampling (DCS) and digitize to extract pulse height and timing
- LSB  $\sim 100\text{e}$ , max. input = 100Ke: 10-bit dynamic range
- Measurement resolution required = a few percent




# “Pipeline” version design

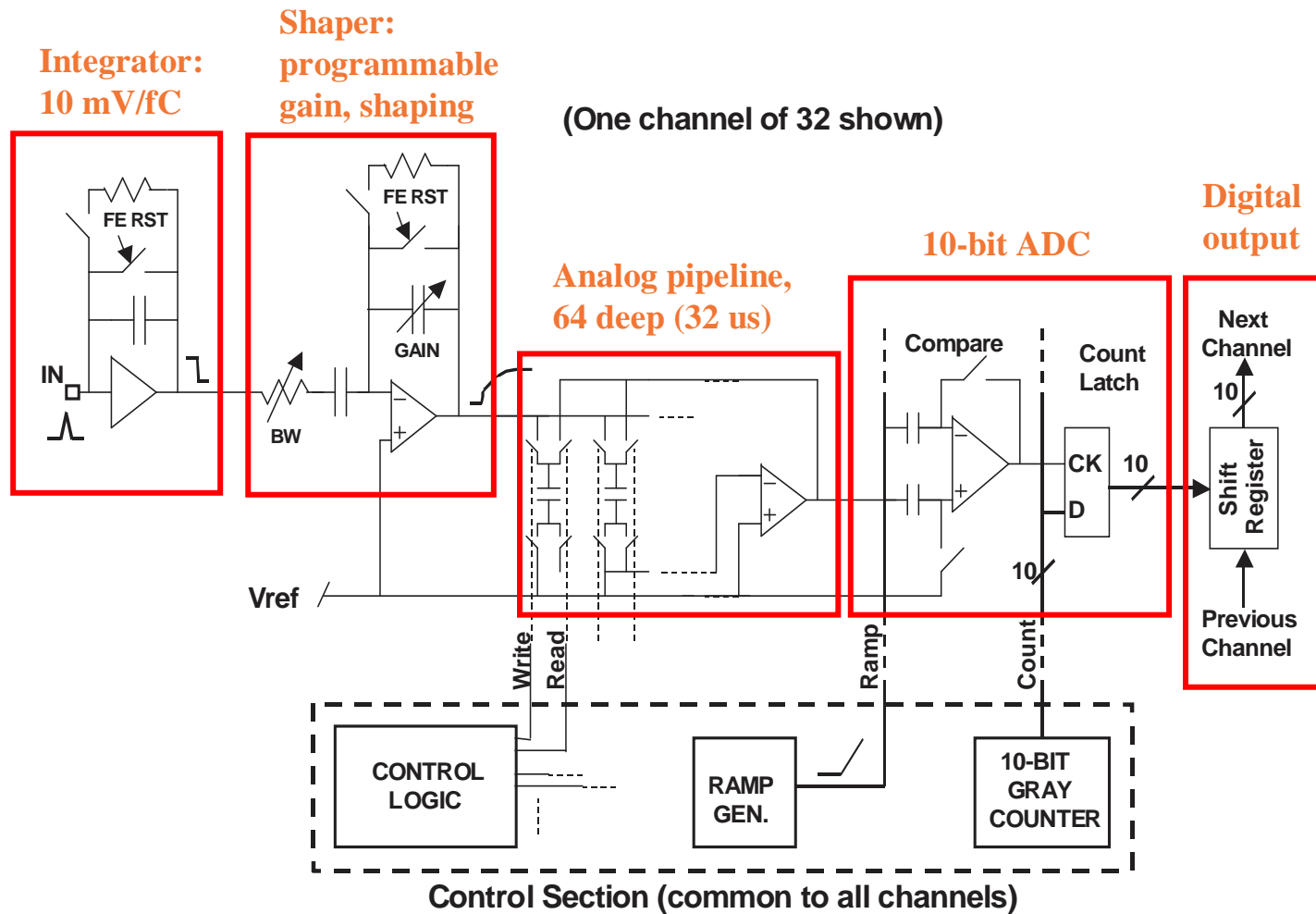
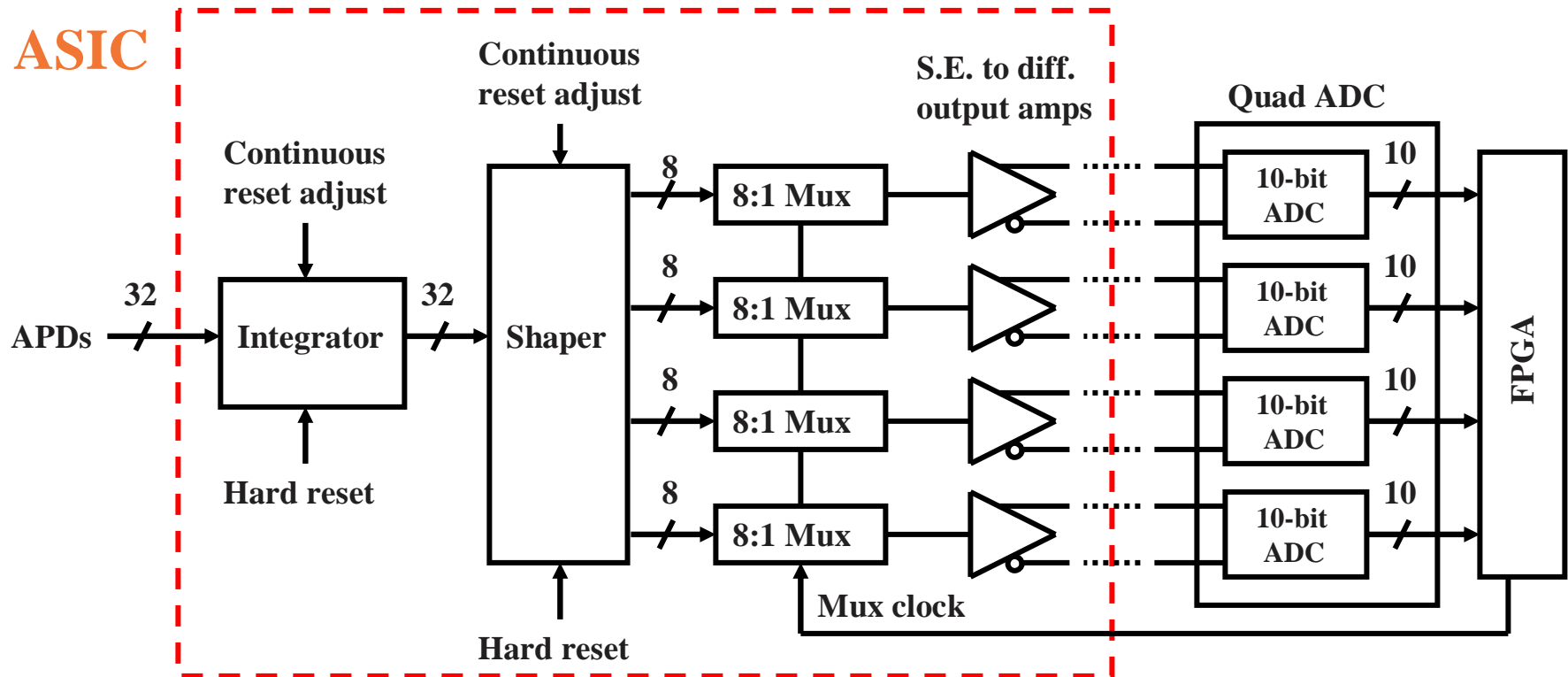
## Alternate ASIC configuration (“Mux” version)

- Would also like to detect supernova neutrino signal (capture 10s of seconds)
- Requires near 100% live time (continuous acquisition and digitization)
- Use four 8:1 analog multiplexers with external ADCs. Multiplex and digitize at  $8 \times [\text{sample freq.}] = 8 \times [1/500\text{ns}] = 16 \text{ MHz}$ . Perform DCS and additional processing digitally in FPGA
- Risk: coupling to low noise front end from continuous digitize/readout




# Which approach for NOvA ?

- **Baseline approach:** “Mux” ASIC with external ADCs, allowing 100% live time. Required: ASIC + Quad ADC + FPGA.
- **Backup approach:** “Pipeline” ASIC, allowing separate acquire/digitize cycles if necessary. Required: ASIC + FPGA.
- **Prototype ASIC:** integrate both approaches on one chip, giving maximum flexibility for optimizing the APD readout strategy. Use TSMC 0.25 micron process.

# NOvA prototype ASIC


Mux version  
analog output

Pipeline version  
digital output

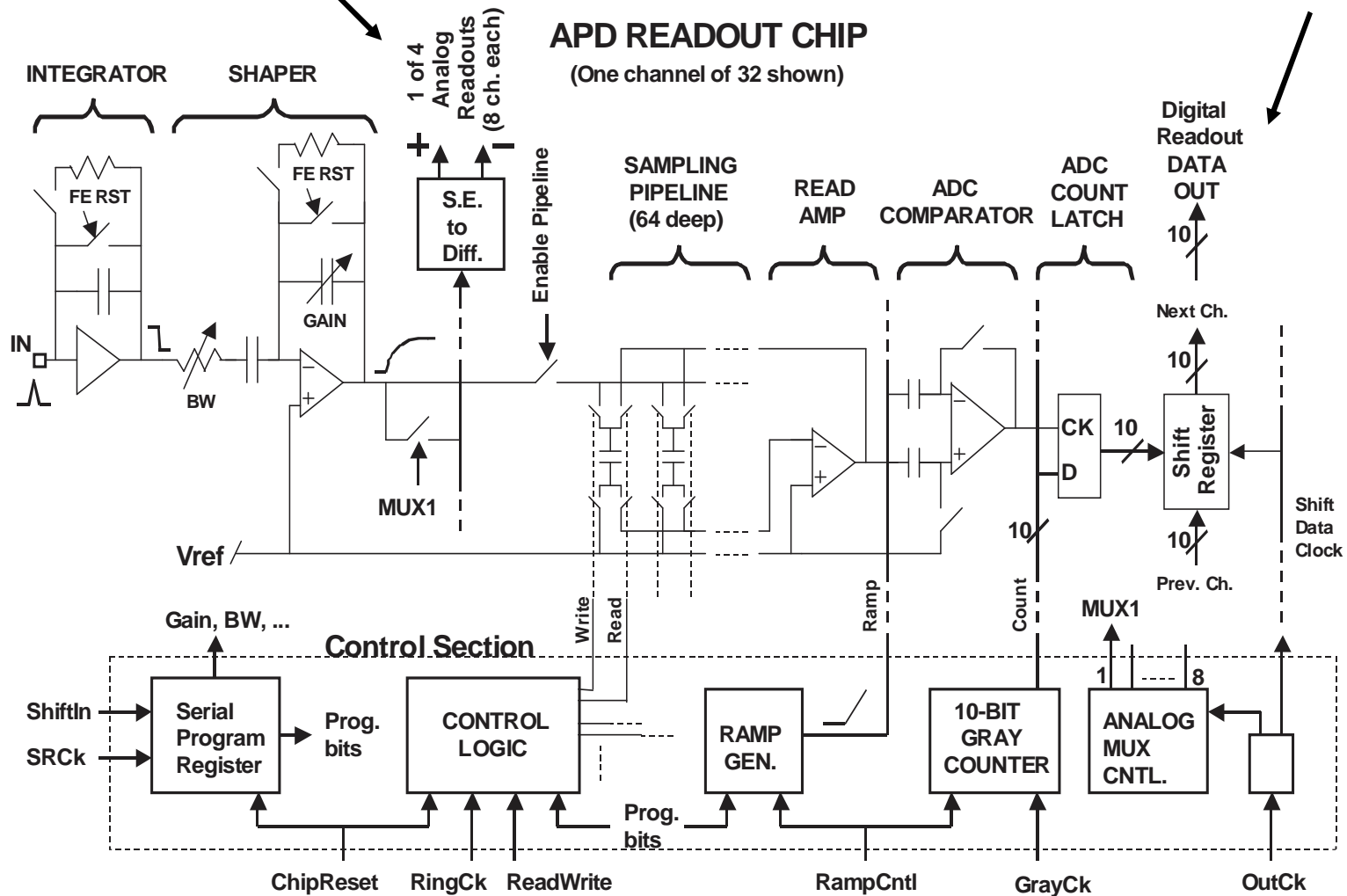
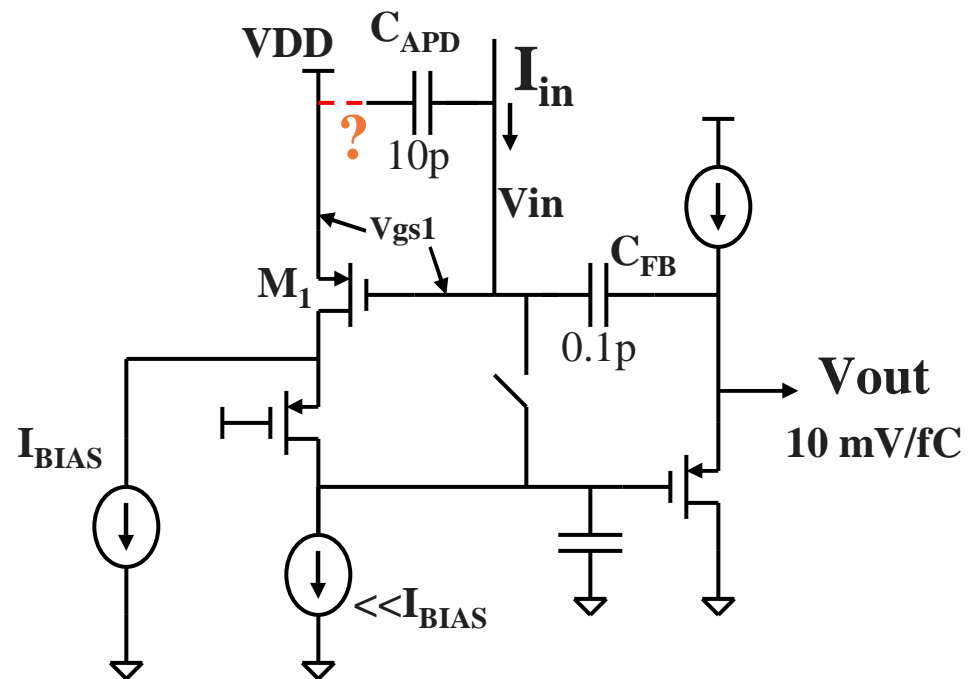
# Integrator

- 1 LSB  $\sim 100e$ : use 10 mV/fC ( $C_{FB} = 0.1\text{pF}$ ), followed by shaper gain (x2-x10)
- 500 ns sample time:  $M_1$  is PMOS to avoid significant  $1/f$  noise contribution.
- $M_1$  (PMOS) source is referred to VDD, not ground.
- Where to refer APD capacitance for best PSRR?
- If  $I_{BIAS}$  is fixed, then  $V_{gs1}$  is constant, so  $\Delta V_{in} = \Delta V_{DD}$ . If  $C_{APD}$  grounded:  
 $\Delta V_{out}/\Delta V_{DD} = \Delta V_{out}/\Delta V_{in} = C_{APD}/C_{FB} = 100$  (disaster!!)
- If  $C_{APD}$  is referred to VDD:
  - Tight input loop (minimizes pickup)
  - $\Delta V_{out}/\Delta V_{DD} = 1$  (better!!)



- But what about  $C_{\text{STRAY}}$  to ground (bond pad, bondwire, etc.)? Ruins PSRR.
- Use  $M_2$  with  $V_{\text{gs}} = V_{\text{DD}}$  to generate  $I_{\text{BIAS}}$ .

Two advantages:

- 1. For a given  $I_{\text{BIAS}}$ , **max.  $V_{\text{gs}2}$  yields min.  $g_{m2}$ , lowest  $M_2$  noise.**
- 2.  $I_{\text{BIAS}}$  changes with  $V_{\text{DD}}$ . Now  $\Delta V_{\text{in}} = (\Delta V_{\text{DD}})[1 - (g_{m2}/g_{m1})]$ .


If  $(C_{\text{STRAY}}/C_{\text{APD}}) = (g_{m2}/g_{m1})$ , then  $\Delta V_{\text{out}} = 0!!$  (to 1<sup>st</sup> order).

- Typically  $(g_{m2}/g_{m1}) \sim 0.05$ :

$M_2$  noise contribution  $\sim 2\%$

Optimum  $C_{\text{STRAY}} \sim 0.5\text{pF}$

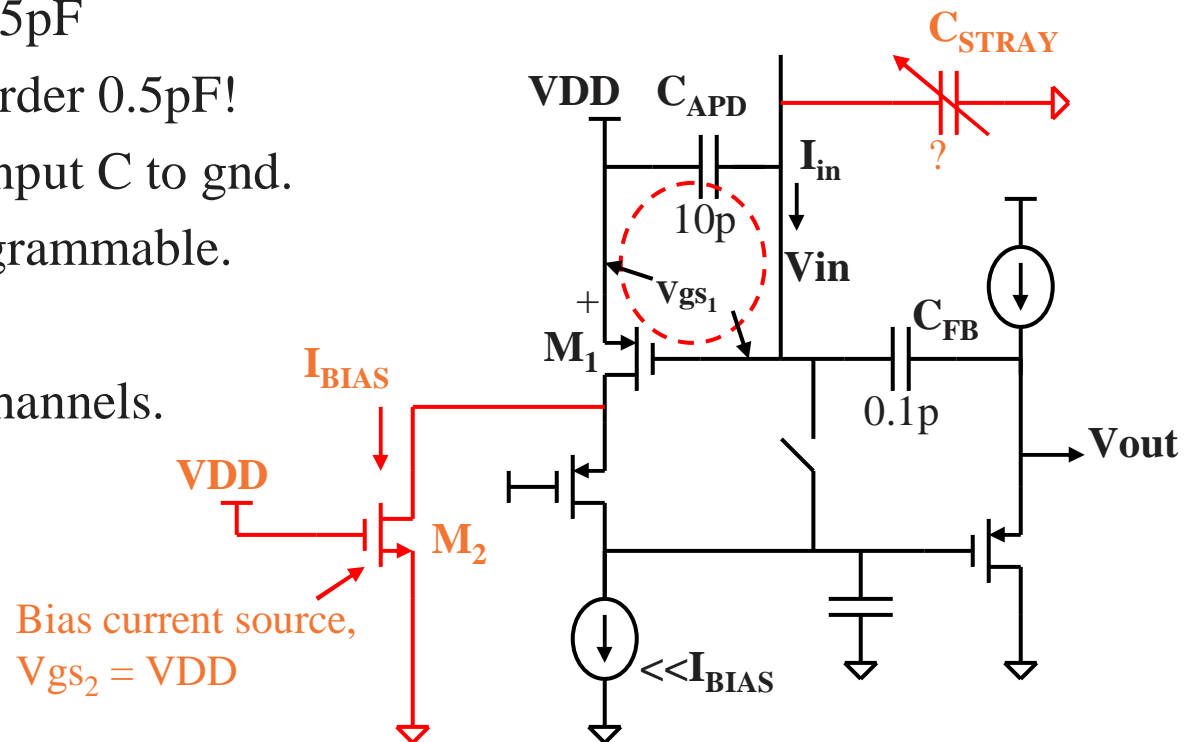
- Unavoidable  $C_{\text{STRAY}}$  is of order  $0.5\text{pF}$ !
- Add small programmable input  $C$  to gnd.
- Make  $I_{\text{BIAS}}$  ( $M_2$  width) programmable.
- Tweak for best PSRR!
- Assumes same  $C$ 's on all channels.




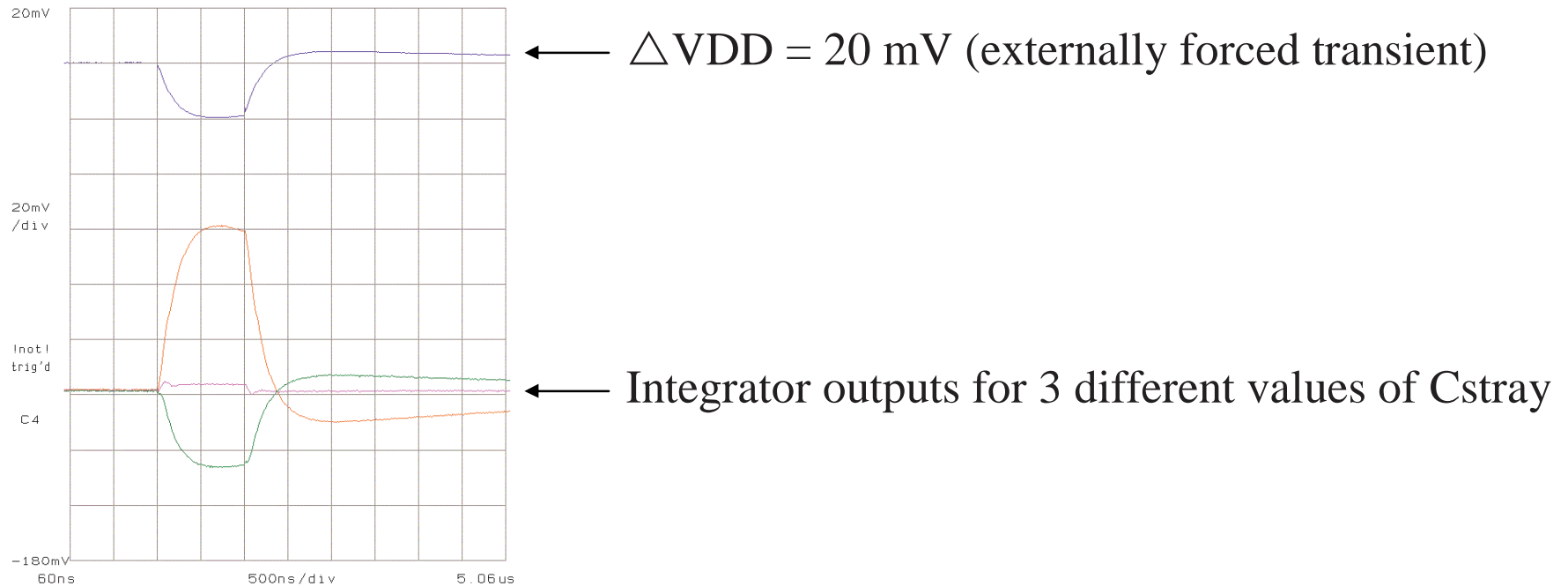
## Integrator output response to VDD transient


$C_{in} = 15 \text{ pF (to VDD)} + C_{stray} \text{ (to gnd, programmable)}$





Tweak C<sub>stray</sub> for best VDD immunity!
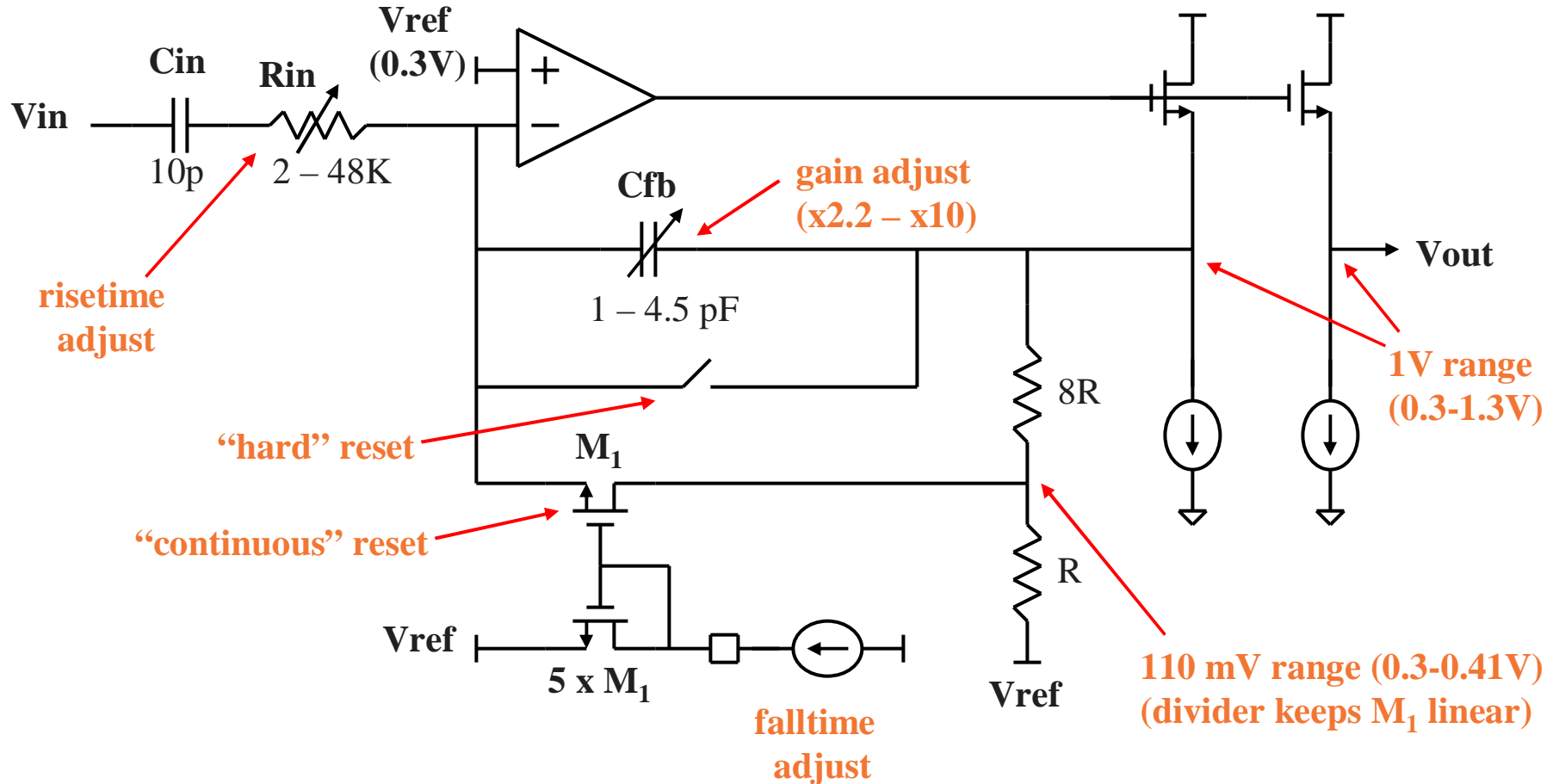
# Shaper

- Risetime set by ( $R_{in}C_{in}$ ), programmable. Not affected by gain setting.
- Voltage gain set by ( $C_{in}/C_{fb}$ ), programmable. Not affected by risetime setting.
- External adjustment for falltime. Falltime affected by gain setting ( $C_{fb}$ ).
- Falltime independent of signal magnitude.




# Shaper output programmable risetime

  


16 settings give risetime from 57 ns to 446 ns

## Shaper output programmable gain

 

8 settings give shaper gain from x2.2 to x10.  
No significant effect on risetime.

## Shaper output with finite fall time

 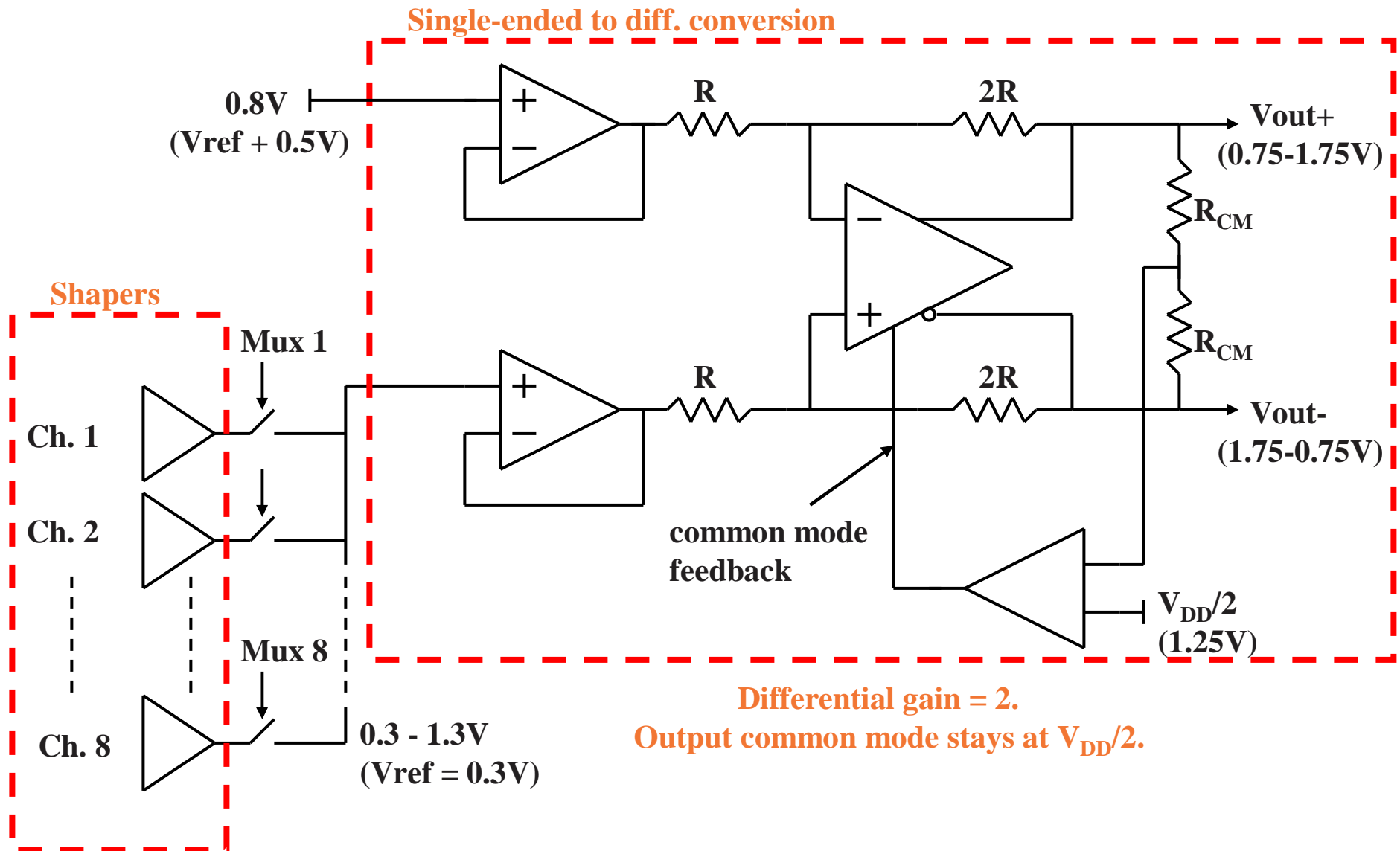

$$\Delta V_{\text{out}} = 1200 \text{ mV}$$

4 values of  $\Delta V_{out}$ :  
120, 300, 600, 1200 mV  
(normalized)

$$\Delta V_{\text{out}} = 120 \text{ mV}$$


(feedback divider gives relatively stable  
faltime for different output amplitudes)

# Mux Version: single-ended shaper output converted to differential output to drive ADC




## S.E. to diff. amplifier response for different amplitudes (scaled)

Vout+ (positive amplifier output)

 

**Completely settled in < 40 ns**

 
## Differential output $[(V_{out+}) - (V_{out-})]$ for max. amplitude (2V)




 
## Multiplexer readout with VDD transient


Variations at integrator outputs (amplified by shaper) appear at mux output.




←  $\Delta VDD = 0.3 \text{ mV}$  (from operating the mux).  
(1 mV/div)

← Tweak Cstray for best integrator immunity!  
Optimum Cstray depends on Cin to VDD.

 
← Mux readout for 3 different programmed  
values of Cstray.  
(10 mV/div)


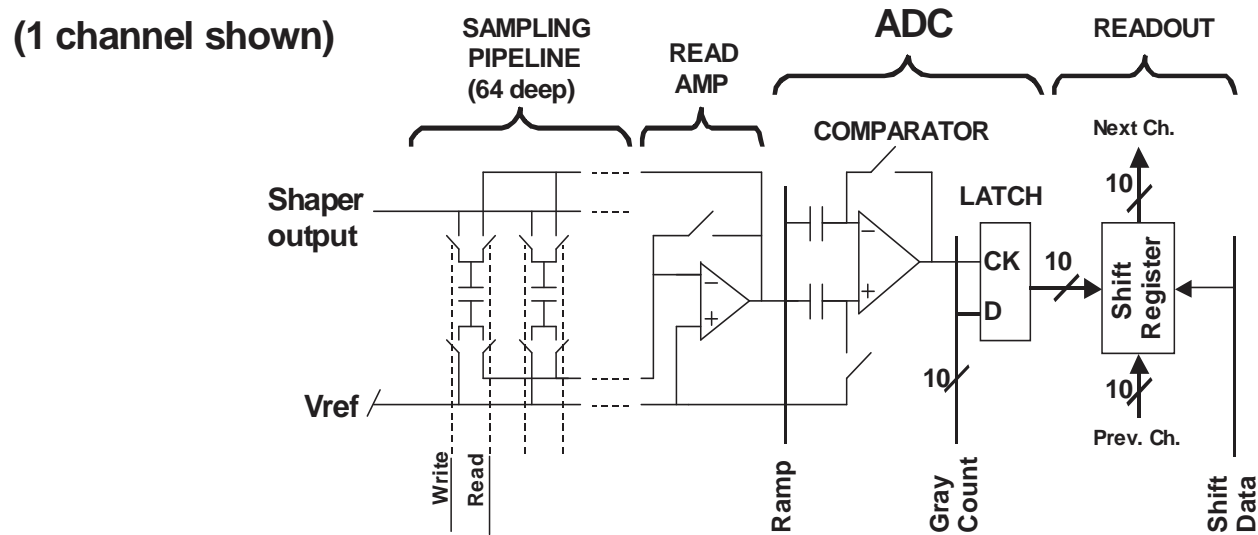
## Pipeline Version: 64 deep pipeline + on-chip multichannel Wilkinson ADC



**Digitize  $\Delta V = (V_2 - V_1)$ :**

 


# Two digitize options

- **Option 1: cell only**

V1 = Read amp reset voltage (Vref) always

V2 = Pipeline cell voltage (Vref + excursion due to shaper output)

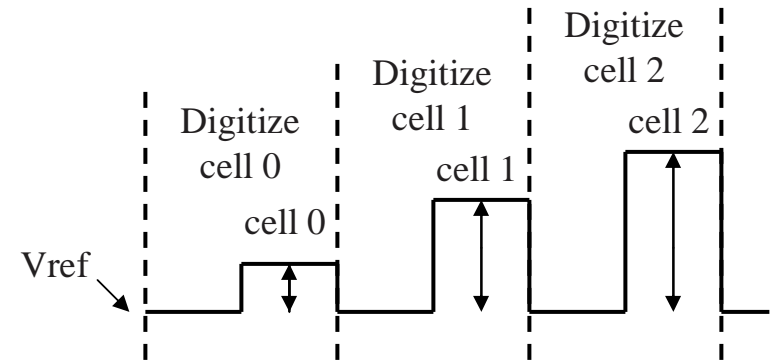**The ADC directly digitizes the shaper signal level sampled by each cell of the pipeline. The signal is always positive with respect to Vref.**




- **Option 2: DCS**

V1 = Pipeline cell (n-1) voltage

V2 = Pipeline cell (n) voltage

 **The ADC digitizes the difference between two neighboring pipeline cell voltages (dual correlated sampling). Continuous shaper reset should not be used, since only positive differences can be digitized.**



## Two acquire/digitize modes

- **Mode 1: Separate acquisition and digitization:**

First acquire signals by filling the pipeline, then stop acquisition.  
Digitize and readout all pipeline cells.

- **Mode 2: Concurrent acquisition and digitization:**

Acquisition and digitization occur simultaneously (with latency).  
Range or resolution must be sacrificed in order to digitize every  
500 ns.

# Progress to date

- The chip is completely functional.
- MUX version: performance is adequate and meets all specs.
- PIPELINE version: only the “Separate acquisition and digitization” mode has been tested. The on-chip ADC digitizes dual correlated samples as desired.
- The DCS digitize option was used to measure noise.
- “Concurrent acquisition and digitization” mode not yet studied. Coupling from digital back end to analog front end???

# Noise Measurements

## Conditions:

- Integrator input transistor bias current = 1mA
- Shaper rise time constant = 206 ns (hard reset, infinite fall time)
- Shaper gain = X10 (integrator + shaper = 100 mV/fC)
- Dual correlated sample ( $t = 1000$  ns)
- Noise downstream from integrator (shaper + ADC) = 41 electrons (for shaper gain = 10). Subtract this noise from the measurement to get only the integrator noise contribution.
- Many different variations of input transistor W/L.

## Integrator Noise Measurements

| W/L      | DCS noise (e)  |
|----------|----------------|
| 880/.32  | 6e + 8.5e/pF   |
| 1200/.32 | 9e + 7.7e/pF   |
| 1540/.32 | 14e + 7.3e/pF  |
| 620/.4   | 7e + 9.4e/pF   |
| 880/.4   | 5e + 8.4e/pF   |
| 1540/.4  | 19e + 7.5e/pF  |
| 620/.6   | 8e + 9.5e/pF   |
| 1540/.6  | 21e + 7.9e/pF  |
| 620/1    | 23e + 10.2e/pF |
| 1540/1   | 49e + 8.4e/pF  |

- Noise slope measurement is accurate
- Noise intercept not as accurate (stray wiring C ~ 7pF subtracted out)

Best: 10 pF noise = 87e  
20 pF noise = 160e

- The measured noise is *lower* than the simulated noise! High confidence in measurements.
- SVX3 chip noise measurements with NMOS input transistor (TSMC 0.25 u) showed “excess” noise at shorter channel lengths (used L = 0.8u). PMOS shows no such behavior – shorter is better (should have tried L = 0.25u!).